

Electronics 1: Chapter 6 figs

Alan Robert Clark

April 19, 2022

Note that the source code for the figs can be seen by clicking the pic. You will need to use your Browser's BACK button to return to this page.

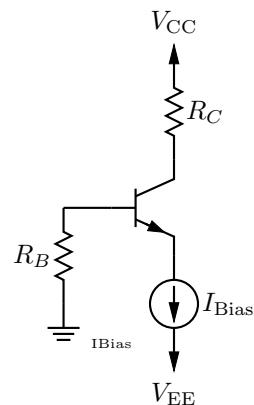


Figure 1: Simple circuit (just looking at biasing) showing Current source biasing

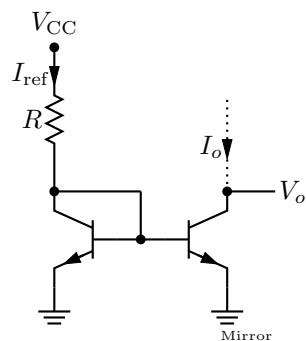


Figure 2: Simple BJT Current Mirror

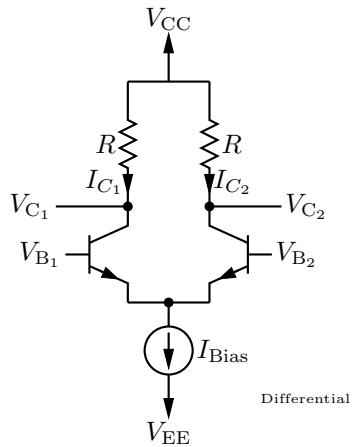


Figure 3: A “long-tailed” differential pair.

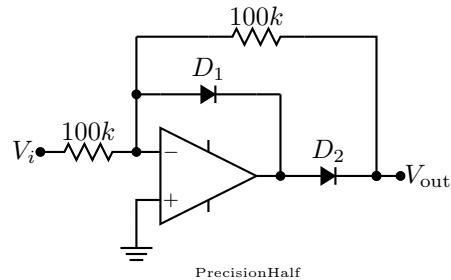


Figure 4: A Precision Half Wave Rectifier.

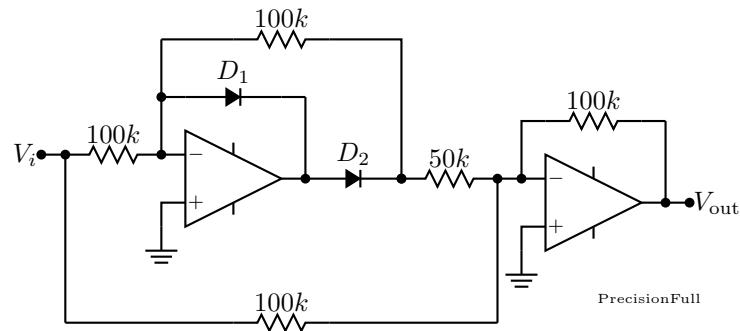


Figure 5: A Full-wave Precision Rectifier

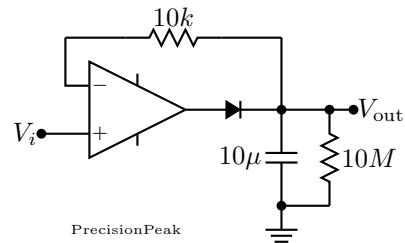


Figure 6: A Precision Peak Detector.

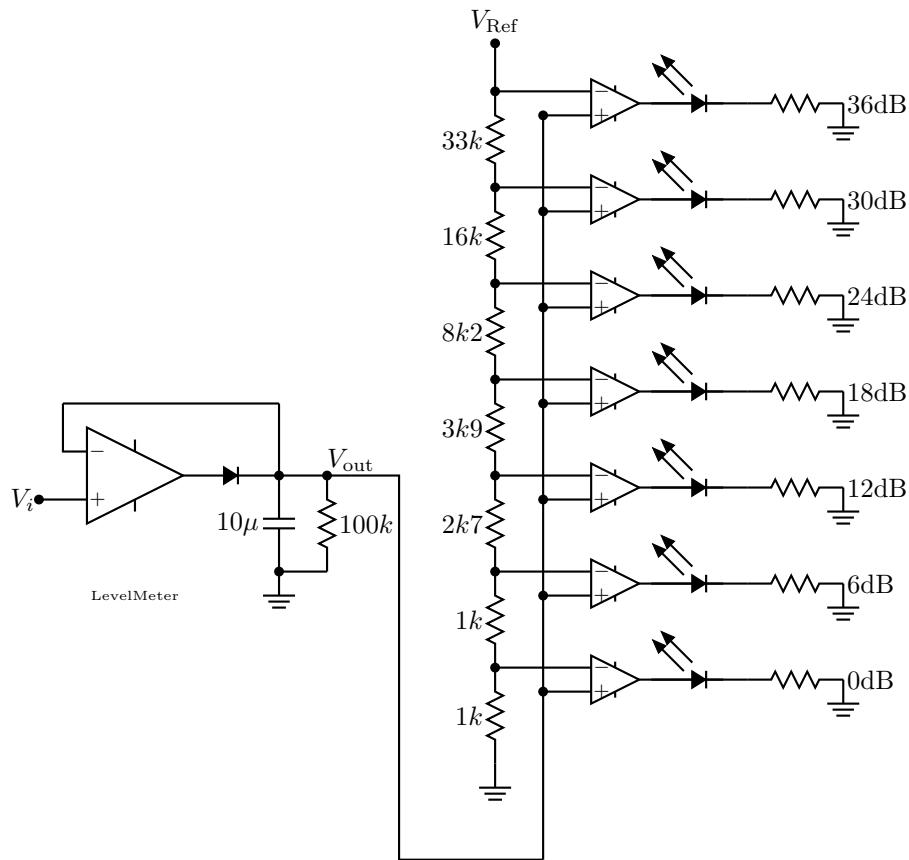


Figure 7: A simple audio “Level Meter” with a string of comparators

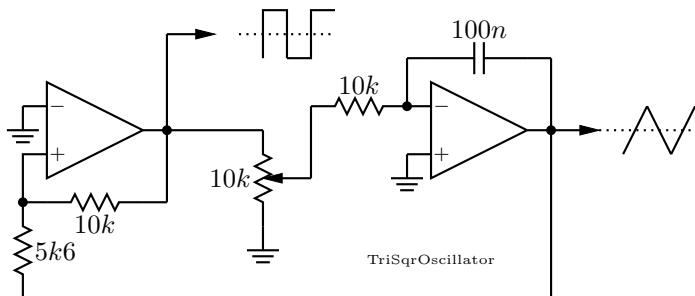


Figure 8: Triangle and Square wave oscillator

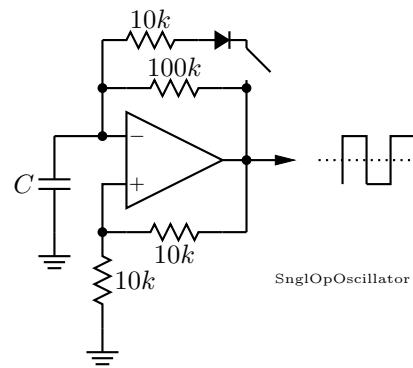


Figure 9: An oscillator constructed around a single OpAmp.

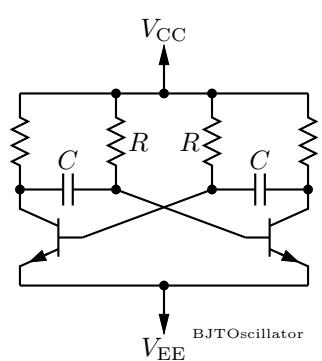


Figure 10: “Classic” BJT Oscillator