

# Electronics 1: Chapter 1 figs

Alan Robert Clark

April 19, 2022

Note that the source code for the figs can be seen by clicking the pic. You will need to use your Browser's BACK button to return to this page.

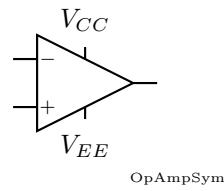


Figure 1: Typical Op-Amp symbol

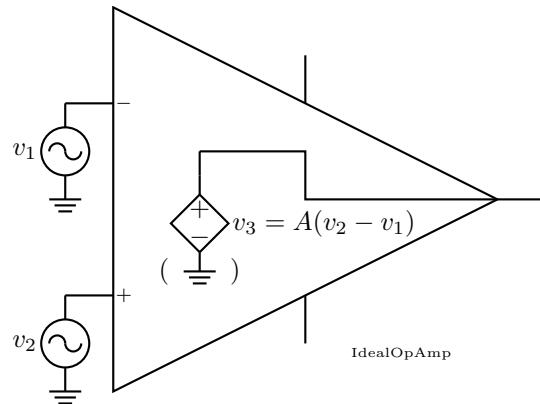


Figure 2: A model of the Ideal Op-Amp

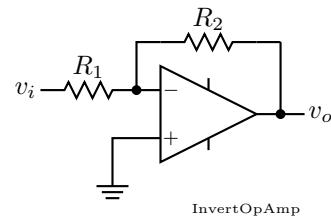


Figure 3: The Inverting configuration

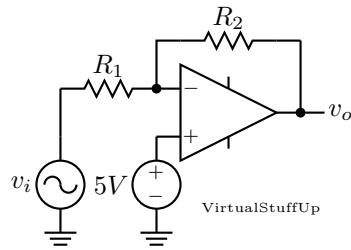


Figure 4: The quest for a Virtual Earth

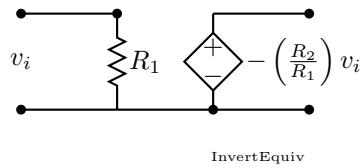


Figure 5: Equivalent circuit of the inverting Op-Amp

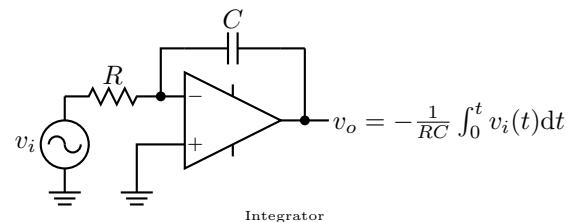


Figure 6: An Integrator configuration.

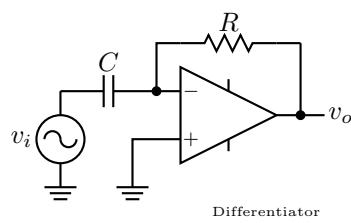


Figure 7: The Differentiator Configuration

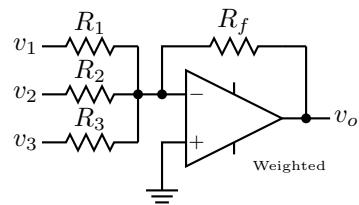


Figure 8: The Weighted Summer

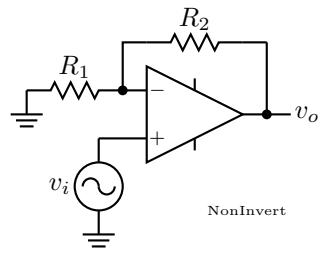


Figure 9: The non-inverting configuration

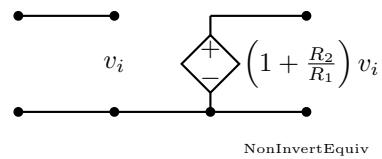


Figure 10: Equivalent circuit of the non-inverting Op-Amp

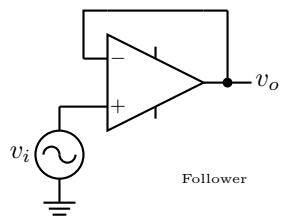


Figure 11: A Unity-gain voltage follower

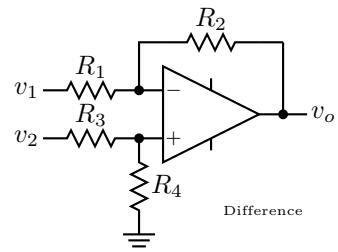


Figure 12: A Difference Amplifier

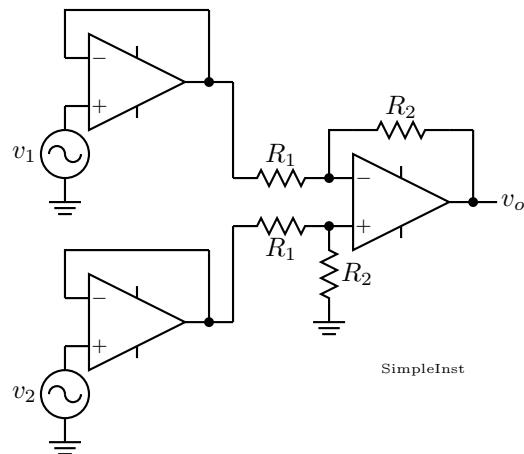


Figure 13: Simple Instrumentation Amplifier

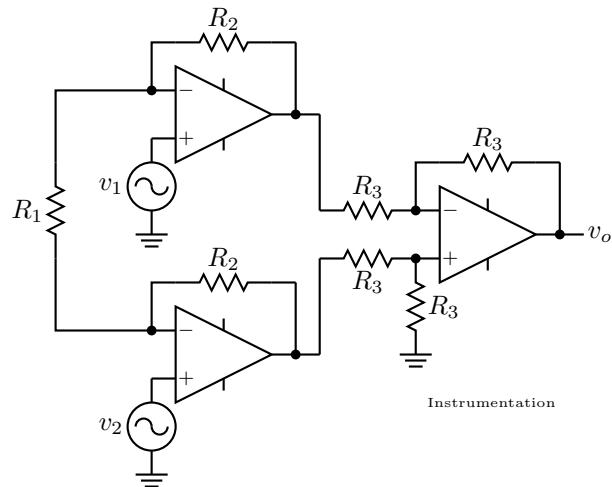


Figure 14: A Standard Instrumentation Amplifier

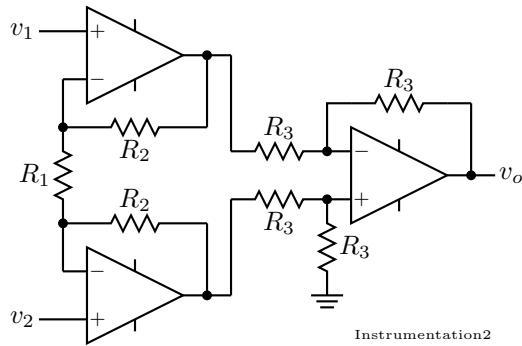


Figure 15: Usual view of Instrumentation Amp

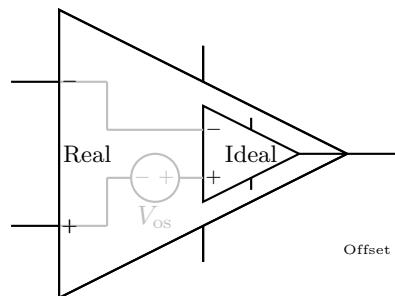


Figure 16: A *Model* of the Offset voltage problem.

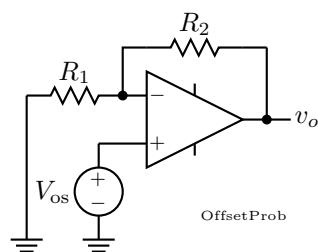


Figure 17: The problem of an offset voltage in closed loop

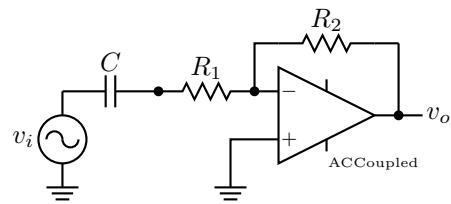


Figure 18: AC-Coupling the amplifier

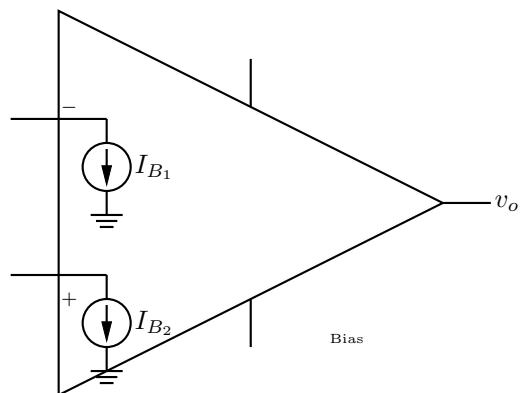


Figure 19: Bias currents modelled as current sinks

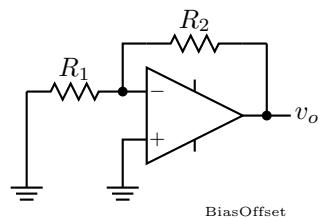


Figure 20: Bias Currents causing an offset voltage.

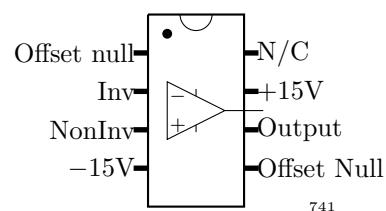


Figure 21: The Pinouts for the 741